

# 计算机体系结构实验 2：32 位单周期处理器设计

15307110200 廖文

## 一、实验要求

1. 仔细阅读教材 7.3 节(P231-239)内容
2. 参考教材 7.6 节(P270-279)代码，完成 MIPS 单周期处理器设计
3. 用教材图 7-60(P276)测试代码测试上述设计
4. 增加 ori、bne 等指令，修改上述 MIPS 单周期处理器：
  - a) 修改 MIPS 处理器原理图(cf 图 7-14)
  - b) 修改主译码器(cf 表 7-3)、ALU 译码器真值表(cf 表 7-2)

修改 Verilog 代码

5. 编写 MIPS 汇编测试代码，测试修改后的 MIPS 处理器

## 二、MIPS 处理器的设计

1. 教材上给出了单周期 MIPS 处理器的设计图如下

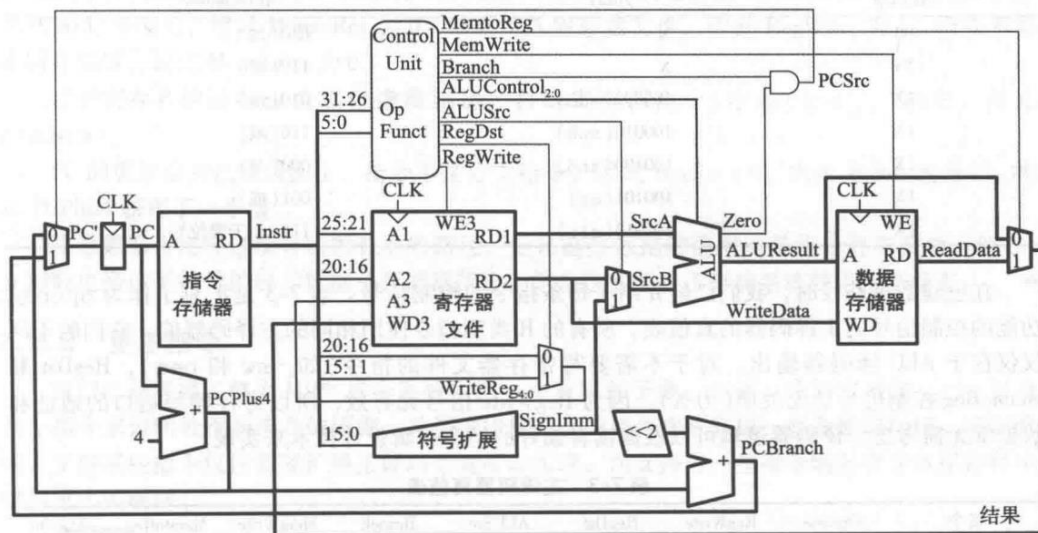


图 7-11 完整的单周期 MIPS 处理器

2. 根据教材所给的处理器代码和测试代码测试上述设计。

其中支持的指令包括

R 型算术/逻辑指令：and, sub, and, or, slt

I 型算术/逻辑指令：addi

存储器指令：lw, sw


分支指令：beq, j

测试代码如下右图所示。


```
# mipstest.asm
# David_Harris@hmc.edu, Sarah_Harris@hmc.edu 31 March 2012
#
# Test the MIPS processor.
# add, sub, and, or, slt, addi, lw, sw, beq, j
# If successful, it should write the value 7 to address 84
```

#	Assembly	Description	Address	Machine
main:	addi \$2, \$0, 5	# initialize \$2 = 5	0	20020005
	addi \$3, \$0, 12	# initialize \$3 = 12	4	2003000c
	addi \$7, \$3, -9	# initialize \$7 = 3	8	2067ffff
	or \$4, \$7, \$2	# \$4 = (3 OR 5) = 7	c	00e22025
	and \$5, \$3, \$4	# \$5 = (12 AND 7) = 4	10	00642824
	add \$5, \$5, \$4	# \$5 = 4 + 7 = 11	14	00a42820
	beq \$5, \$7, end	# shouldn't be taken	18	10a7000a
	slt \$4, \$3, \$4	# \$4 = 12 < 7 = 0	1c	0064202a
	beq \$4, \$0, around	# should be taken	20	10800001
	addi \$5, \$0, 0	# shouldn't happen	24	20050000
around:	slt \$4, \$7, \$2	# \$4 = 3 < 5 = 1	28	00e2202a
	add \$7, \$4, \$5	# \$7 = 1 + 11 = 12	2c	00853820
	sub \$7, \$7, \$2	# \$7 = 12 - 5 = 7	30	00e23822
	sw \$7, 68(\$3)	# [80] = 7	34	ac670044
	lw \$2, 80(\$0)	# \$2 = [80] = 7	38	8c020050
	j end	# should be taken	3c	08000011
	addi \$2, \$0, 1	# shouldn't happen	40	20020001
end:	sw \$2, 84(\$0)	# write mem[84] = 7	44	ac020054

从命令行的输出可以看到，程序成功执行。

 

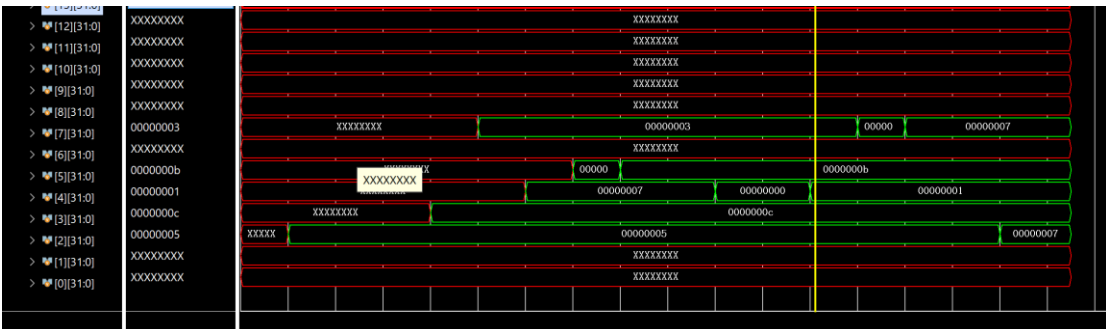为了更加直观的展示测试程序执行期间处理器的状态，我们在模拟的结果中输出寄存器的值如下。



三、增加指令

考虑增加 ori 和 bne 指令。首先在教材附录 1 中找到这两条指令的描述。

001101(13)	ori rt, rs, imm	立即数或	[rt] = [rs]   ZeroImm
000101(5)	bne rs, rt, label	如果不相等则转移	if ([rs] != [rt]) PC = BTA

已经支持的两条相似的指令为

001000(8)	addi rt, rs, imm	立即数加法	[rt] = [rs] + SignImm
000100(4)	beq rs, rt, label	如果相等则转移	if ([rs] == [rt]) PC = BTA

ori 指令在 addi 指令的基础上进行修改即可，不需要增加额外的部件和标志位。  
bne 指令在 beq 指令的基础上进行修改，我们增加了一个标志位 bne，标识该分支指令在连个寄存器不相同的时候进行跳转。修改后的部件的代码如下。  
主译码器的真值表与 ALU 译码器真值表这里没有画出，对真值表的逻辑的修改见代码中背景为黄色的部分。

```
//decide the alu control bit given the funct field and aluop field of
the instruction
//combinational logic
module aludec(
    input logic [5:0] funct,
    input logic [1:0] aluop,
    output logic [2:0] alucontrol);

    always_comb
        case(aluop)
            2'b00: alucontrol <= 3'b010; // add (for lw/sw/addi) end;
```

```

        2'b01: alucontrol <= 3'b110; // sub (for beq) architecture
behave of aludec is
        2'b11: alucontrol <= 3'b001;
        default: case(funct) // R-type instructions begin
            6'b100000: alucontrol <= 3'b010; // add process(all )
begin
            6'b100010: alucontrol <= 3'b110; // sub case aluop is
            6'b100100: alucontrol <= 3'b000; // and when "00" =>
alucontrol <= "010" ; -- add (for lw/sw/addi )
            6'b100101: alucontrol <= 3'b001; //or when "01" =>
alucontrol <= "110"; -- sub (for beq)
            6'b101010: alucontrol <= 3'b111; // sit when others =>
case funct is - R-type instructions
            default: alucontrol <= 3'bxxx; // ??? when "100000" =>
alucontrol <= "010"; - add
            endcase // when "100010" => alucontrol <= "110"; - sub
            endcase // when "100100" => alucontrol <= "000"; -- and
endmodule

//decide controls according to the opcode of instruction
//combinational logic
module maindec(
    input logic [5:0] op,
    output logic memtoreg, memwrite, //
    output logic branch, bne, alusrc,
    output logic regdst, regwrite,
    output logic jump,
    output logic [1:0] aluop
);

    logic [9:0] controls;

    assign {regwrite, regdst, alusrc, branch, bne, memwrite,
memtoreg, jump, aluop} = controls;

    always_comb
        case(op)
            6'b000000: controls <= 10'b1100000010; // RTYPE
            6'b100011: controls <= 10'b1010001000; // LW
            6'b101011: controls <= 10'b0010010000; // SW
            6'b000100: controls <= 10'b0001000001; // BEQ
            6'b000101: controls <= 10'b0001100001; // BNE
            6'b001000: controls <= 10'b1010000000; // ADDI
            6'b001101: controls <= 10'b1010000011; // ORI

```

```

        6'b000010: controls <= 10'b00000000100; // J
        default: controls <= 10'bxxxxxxxx; // illegal op
    endcase
endmodule

//combinational logic
//parse the instruction and decide the params of the datapath
module controller(
    input logic [5:0] op, funct,
    input logic zero,
    output logic memtoreg, memwrite,
    output logic pcsrc, alusrc,
    output logic regdst, regwrite,
    output logic jump,
    output logic [2:0] alucontrol);

    logic [1:0] aluop;
    logic branch;
    logic bne;

    maindec md(op, memtoreg, memwrite, branch, bne, alusrc, regdst,
regwrite, jump, aluop);
    aludec ad(funct, aluop, alucontrol );

    assign pcsrc = branch & (bne^zero);

endmodule

```

我们修改后的测试代码如下，其中使用了 ori 和 bne 指令。

```

RAM[0] = 32'h20020004;
RAM[1] = 32'h20030008;
RAM[2] = 32'h34420001; //ori $2 1
RAM[3] = 32'h34630004; //ori $3 4
RAM[4] = 32'h2067fff7;
RAM[5] = 32'h00e22025;
RAM[6] = 32'h00642824;
RAM[7] = 32'h00a42820;
RAM[8] = 32'h10a7000a;
RAM[9] = 32'h0064202a;
RAM[10] = 32'h10800001;
RAM[11] = 32'h20050000;
RAM[12] = 32'h00e2202a;
RAM[13] = 32'h00853820;
RAM[14] = 32'h00e23822;

```

```

RAM[15] = 32'hac670044;
RAM[16] = 32'h8c020050;
RAM[17] = 32'h14440001;//bne $2, $4, #end
RAM[18] = 32'h20020001;
RAM[19] = 32'hac020054;

```

模拟后的命令行输出如下，表明模拟成功。

```

Tcl Console  x Messages  Log
Type a Tcl command here

op:05, jump:0, alucontrol:110
Simulation succeeded
$stop called at time : 195 ns : File "C:/Users/12565/Desktop/2019-2020-spring/computer architecture laboratory/lab_2/lab_2.srcs/sources_1/new/mips.sv" Line 344
INFO: [USF-XSim-96] XSim completed. Design snapshot 'testbench_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
launch_simulation: Time (s): cpu = 00:00:05 ; elapsed = 00:00:09 . Memory (MB): peak = 1858.953 ; gain = 0.000

```

寄存器的值为

